

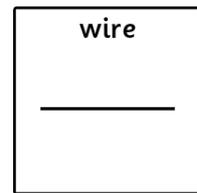
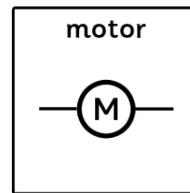
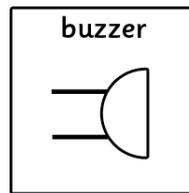
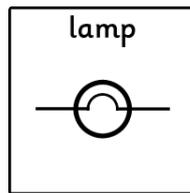
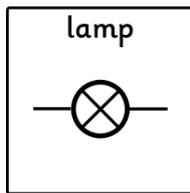
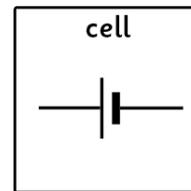
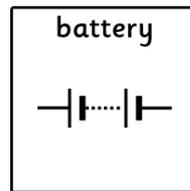
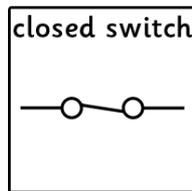


Electric Circuits

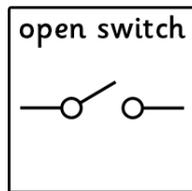Electricity flows in a circuit from the negative pole of a battery to its positive pole. The flow of electricity creates an electric current. There is a symbol to represent each component in an electrical circuit.



Label the circuit below.

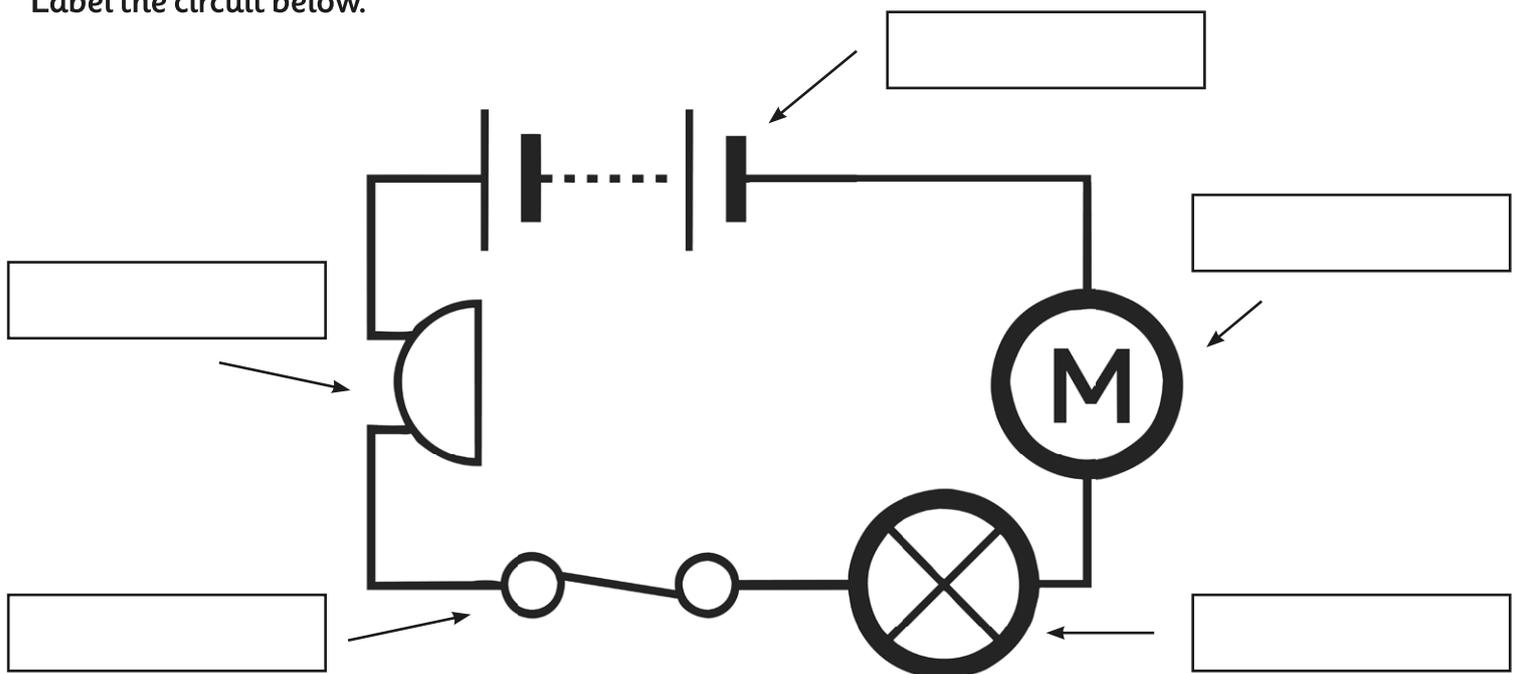


Complete the sentences.

The electric current leaves the _____ and passes through the _____. It then travels through the _____, next through the _____ and finally through the _____ before returning to the battery.

Electric Circuits Answers

Label the circuit below.

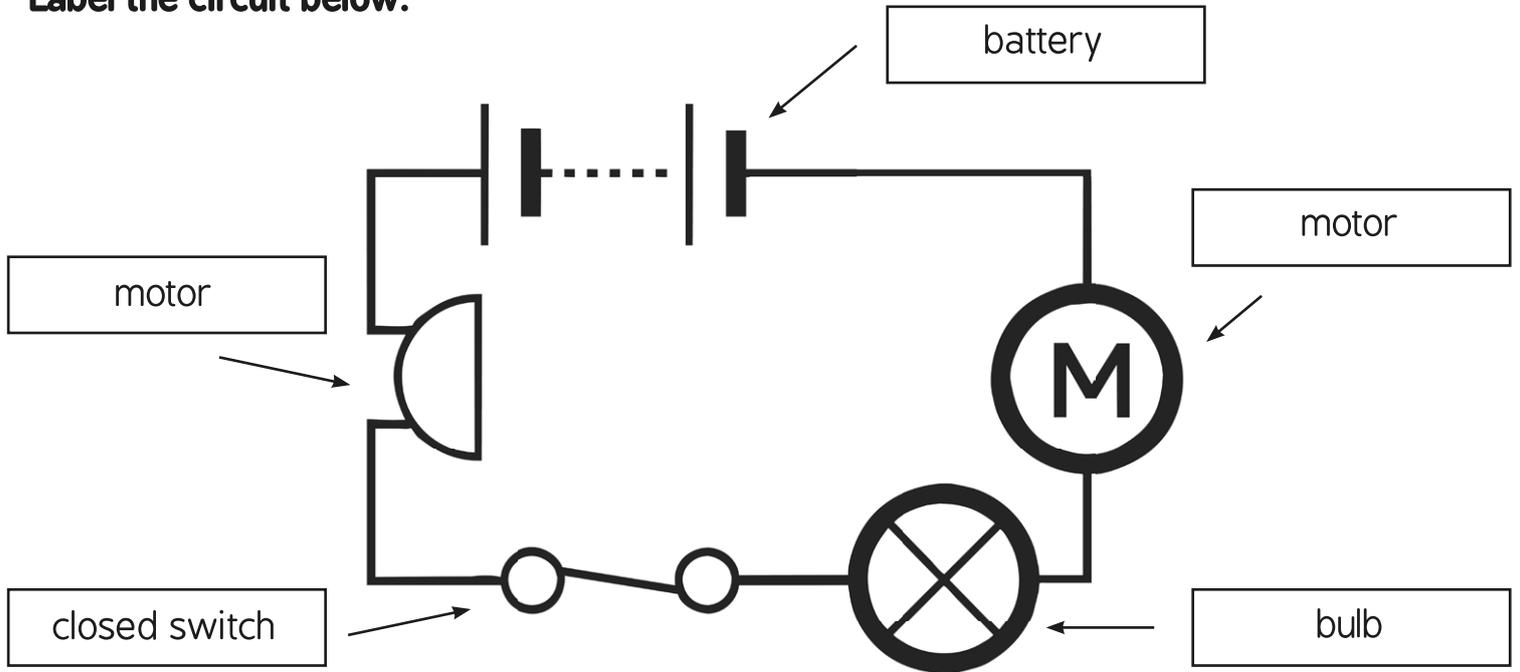

Complete the sentences.

The electric current leaves the battery and passes through the motor.
It then travels through the bulb, next through the closed switch and finally
through the motor before returning to the battery.